

# CS 325 Homework 5 Solutions

Ahmad Jawid Karimi

10/5/2025

## 1. Converting to Standard SOP Form

(a)  $F(A, B, C) = \bar{A}B + C$

$$\begin{aligned}\bar{A}B &= \bar{A}B(C + \bar{C}) = \bar{A}BC + \bar{A}B\bar{C} \\ C &= C(A + \bar{A})(B + \bar{B}) = C(AB + A\bar{B} + \bar{A}B + \bar{A}\bar{B}) \\ &= ABC + A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}C \\ F(A, B, C) &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}C + ABC \\ &= \sum m(1, 2, 3, 5, 7)\end{aligned}$$

(b)  $F(A, B, C) = AB + BC + B$

$$\begin{aligned}F(A, B, C) &= B + AB + BC = B \quad (\text{by absorption}) \\ B &= B(A + \bar{A})(C + \bar{C}) = (AB + \bar{A}B)(C + \bar{C}) \\ &= ABC + A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}C \\ &= \sum m(2, 3, 6, 7)\end{aligned}$$

(c)  $F(A, B, C) = \bar{A}B + AC + \bar{A}C$

$$\begin{aligned}F(A, B, C) &= \bar{A}B + AC + \bar{A}C = \bar{A}B + C(A + \bar{A}) = \bar{A}B + C \\ &= \sum m(1, 2, 3, 5, 7) \quad (\text{same as part a})\end{aligned}$$

## 2. Deriving SOP, POS, and Logic Diagram

Truth table:

A	B	C	F	Minterm	Maxterm
0	0	0	1	$m_0$	
0	0	1	0		$M_1$
0	1	0	1	$m_2$	
0	1	1	0		$M_3$
1	0	0	0		$M_4$
1	0	1	1	$m_5$	
1	1	0	0		$M_6$
1	1	1	1	$m_7$	


### (a) Standard SOP Expression

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}C + ABC = \sum m(0, 2, 5, 7)$$

### (b) Standard POS Expression

$$F = (A + B + \bar{C}) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + B + C) \cdot (\bar{A} + \bar{B} + C) = \prod M(1, 3, 4, 6)$$

### (c) Logic Gate Diagram for POS

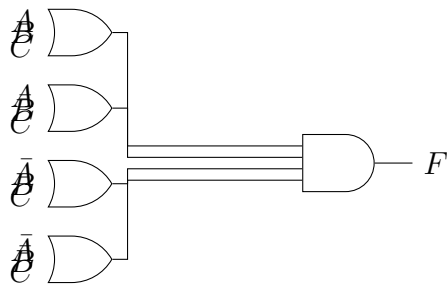

### 3. Karnaugh Map Creation and Derivation

#### K-map from Truth Table

	$C = 0$	$C = 1$
$AB = 00$	1	0
$AB = 01$	1	0
$AB = 11$	0	1
$AB = 10$	0	1

#### Simplified SOP from K-map

Groups of 1's:  $m_0, m_2$  group:  $\bar{A}\bar{C}$  and  $m_5, m_7$  group:  $AC$

$$F = \bar{A}\bar{C} + AC$$


#### Simplified POS from K-map

Groups of 0's:  $M_1, M_3$ :  $\bar{A}C$  and  $M_4, M_6$ :  $A\bar{C}$

$$F = (\bar{A} + C)(A + \bar{C})$$

### 4. 4-Bit Ripple Carry Adder Analysis

$A = 1101, B = 0111, C_{in} = 0$

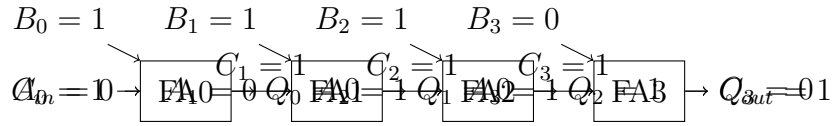

Calculation:

- LSB:  $A_0 = 1, B_0 = 1, C_{in} = 0 \rightarrow Sum = 0, C_{out} = 1$
- Bit1:  $A_1 = 0, B_1 = 1, C_{in} = 1 \rightarrow Sum = 0, C_{out} = 1$
- Bit2:  $A_2 = 1, B_2 = 1, C_{in} = 1 \rightarrow Sum = 1, C_{out} = 1$
- Bit3:  $A_3 = 1, B_3 = 0, C_{in} = 1 \rightarrow Sum = 0, C_{out} = 1$

Final:  $Q = 0100, C_{out} = 1$

## 5. Binary Subtractor Circuit

To modify a 4-bit binary adder to perform subtraction  $A - B$  using two's complement:

1. Invert each bit of  $B$  (find  $\bar{B}$ )
2. Set  $C_{in} = 1$  for the LSB adder

This computes:  $A + (\bar{B} + 1) = A + (\text{two's complement of } B) = A - B$

